

Chapter 3 Smith chart analysis

3.1 Introduction

Smith chart ($Z \rightarrow \Gamma$) and its properties

3.2 Using the Smith chart

7 examples

3.3 Short-circuit shift method

find Z_L from VSWR and minima shift distance


3.4 Impedance matching techniques

$\lambda/4$ transformer, single-stub tuner


3.5 Smith chart radially scaled parameters

3.1 Introduction

Smith chart : conformal map rectangular plot of $z = Z/Z_o = r + jx$ on the polar plot of $\Gamma = |\Gamma|e^{j\angle\Gamma} = \Gamma_r + j\Gamma_i$, $|\Gamma| \leq 1$, $-180^\circ \leq \angle\Gamma \leq 180^\circ$

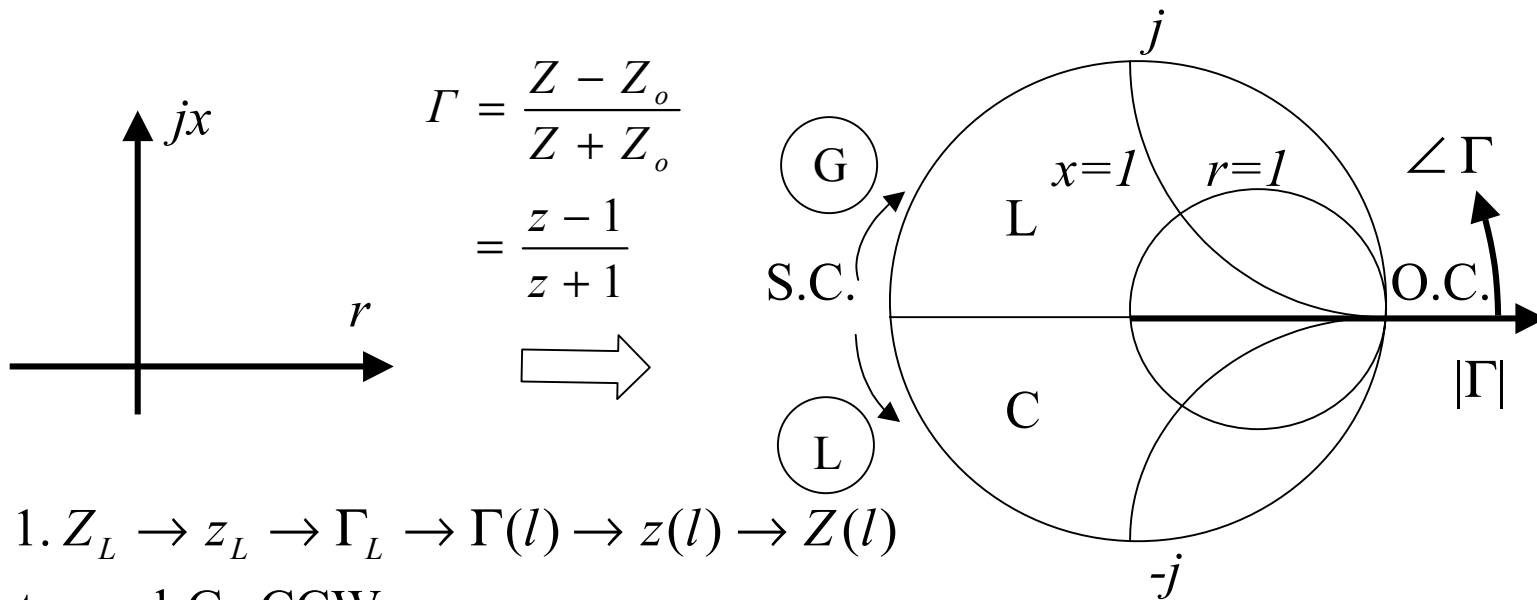

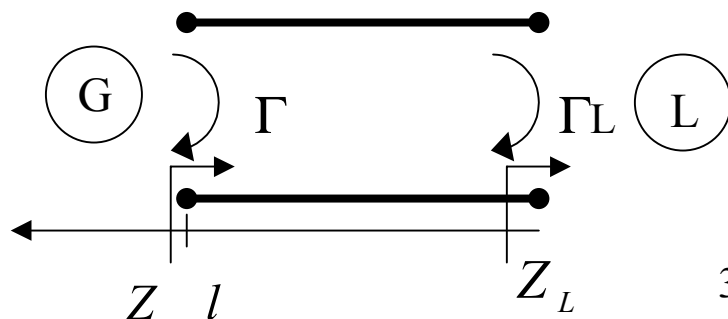1. $Z_L \rightarrow z_L \rightarrow \Gamma_L \rightarrow \Gamma(l) \rightarrow z(l) \rightarrow Z(l)$
toward G : CCW





$$\Gamma(l) \equiv \frac{V^-(l)}{V^+(l)}$$


$$= \frac{V_o^- e^{-j\beta l}}{V_o^+ e^{j\beta l}} = \Gamma_L e^{-j2\beta l}$$

微波工程講義

IMPEDANCE OR ADMITTANCE COORDINATES

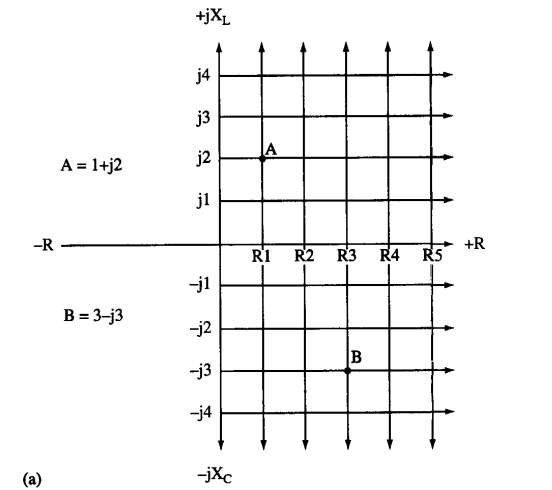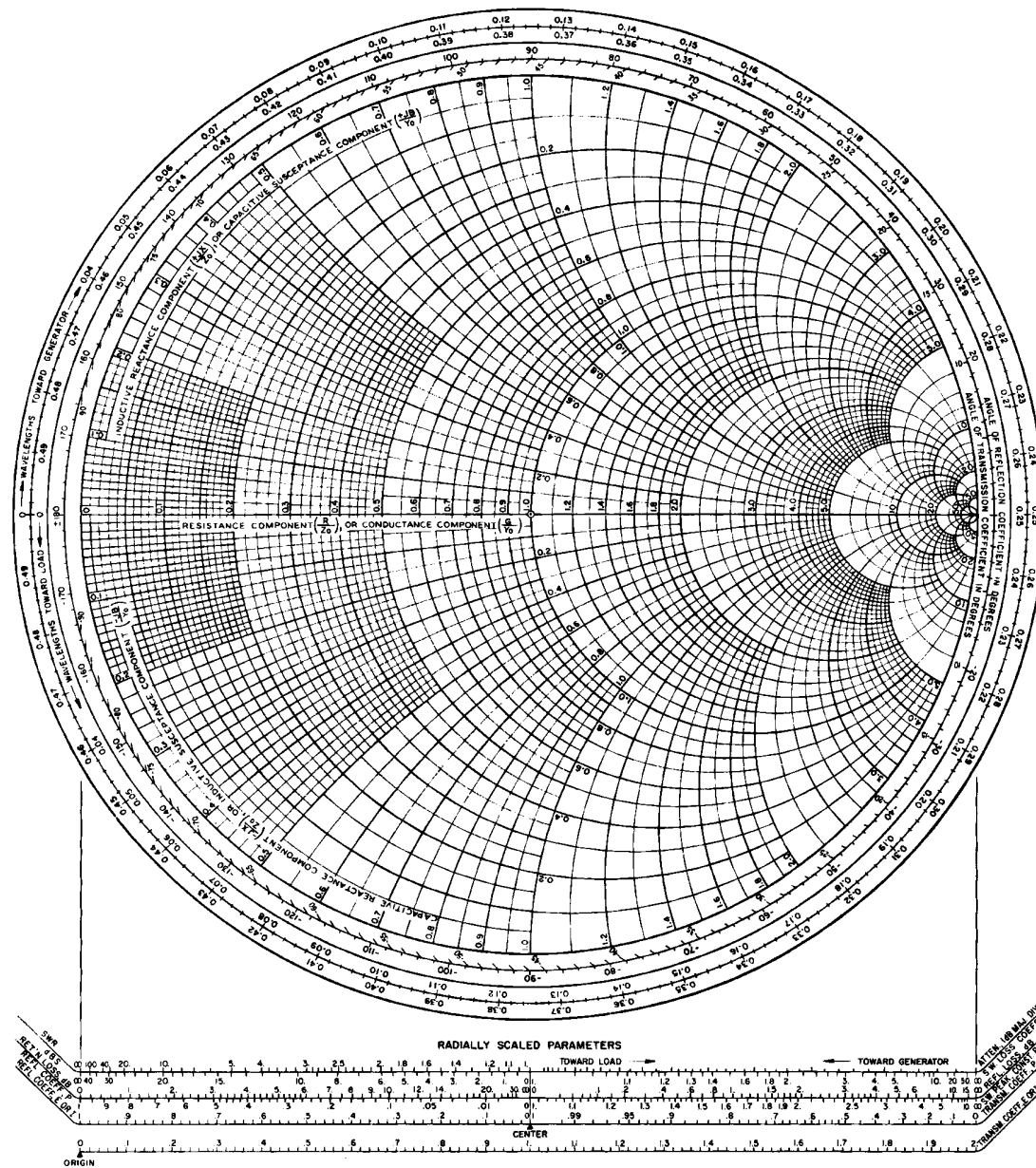


(a)

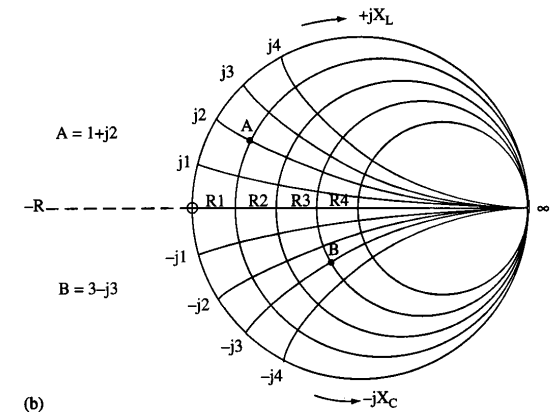


(b)

微波工程講義

2. r - circle \perp x - circle

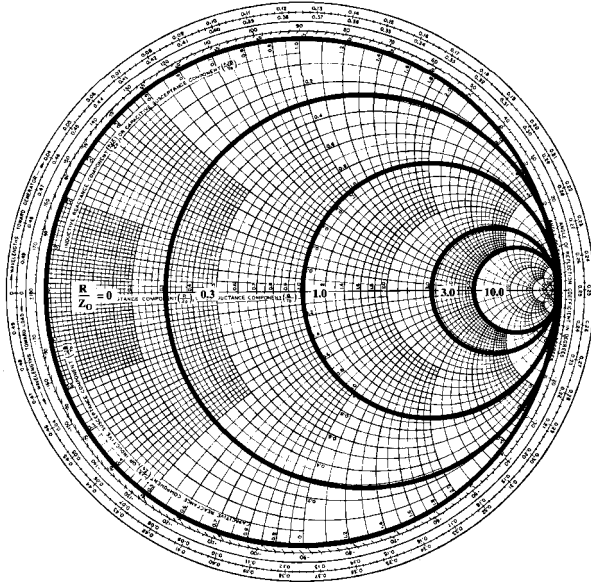

constant r-circle

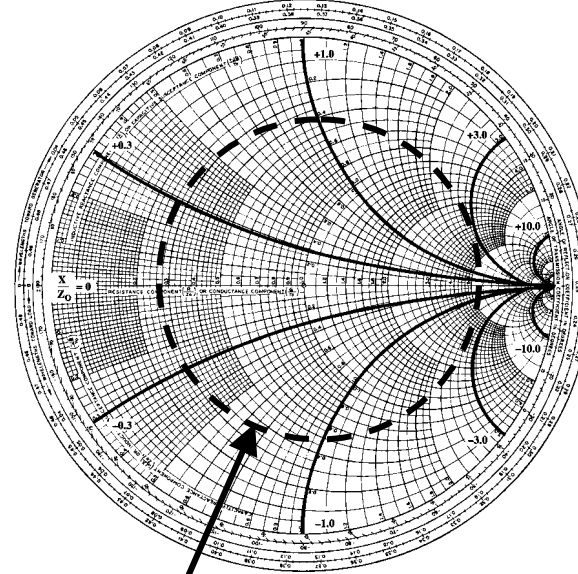

constant x-circle

$$3. VSWR = r_{\max} = \frac{R_{\max}}{Z_o} = \frac{1}{r_{\min}} = \frac{Z_o}{R_{\min}}$$

$$4. y = z^{-1} \rightarrow \angle \Gamma + 180^\circ$$

$$\therefore \Gamma = \frac{Z - Z_o}{Z + Z_o} = \frac{z - 1}{z + 1}, \Gamma' = \frac{z^{-1} - 1}{z^{-1} + 1} = \frac{1 - z}{1 + z} = -\Gamma$$


constant $|\Gamma|$ -circle or
constant VSWR-circle

$$5. l = \lambda / 2 \rightarrow 360^\circ$$

3-4

微波工程講義

6. Ex. points A-G

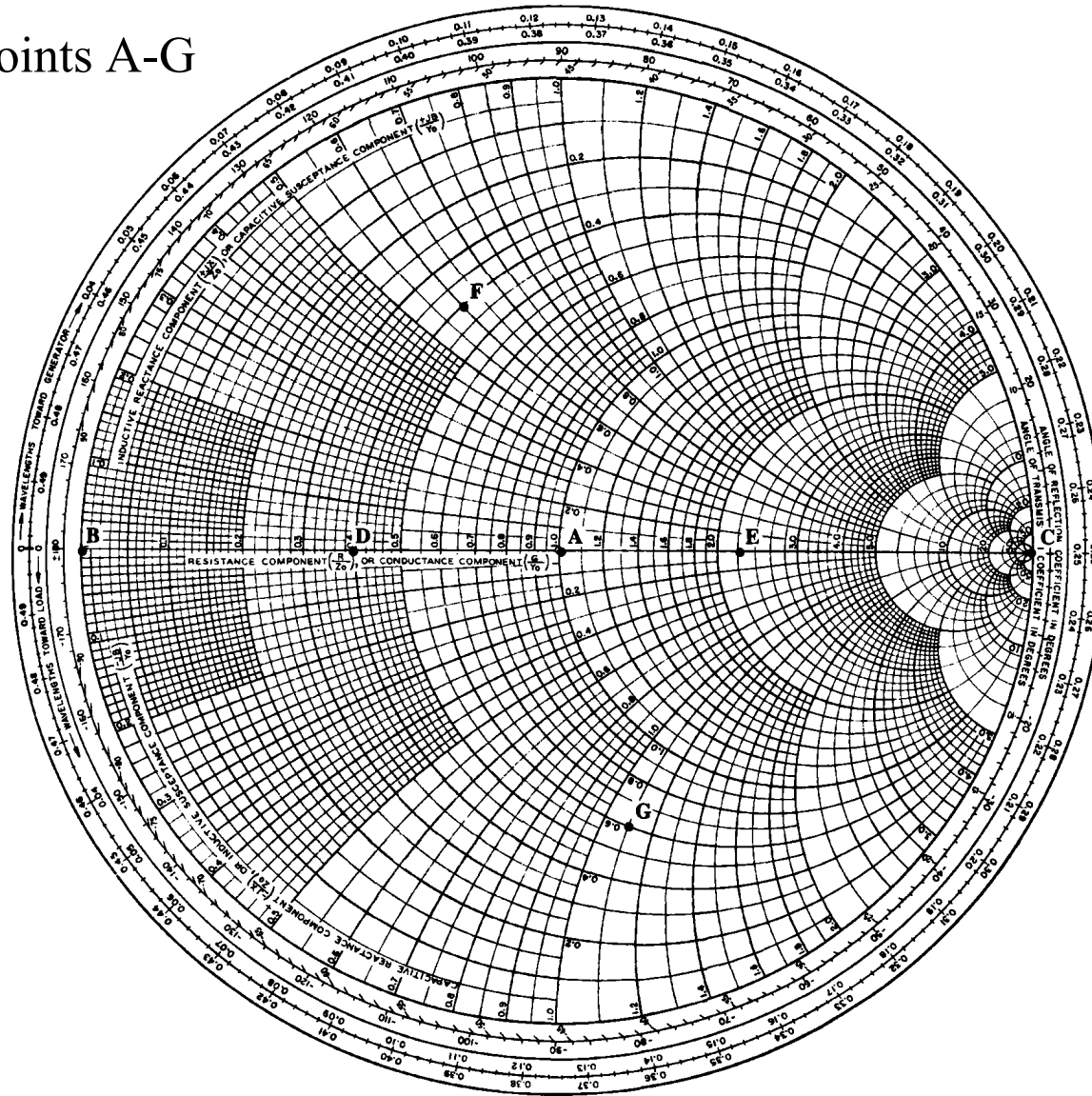


3.2 Using the Smith chart

1. Examples to solve the transmission line problems:

- Ex.1 plot load impedance Z_L
- Ex. 2, 3, 4, 5, 7
given $Z_L \rightarrow$ determine Γ , VSWR, Z_{in} , T (transmission coefficient), RL, Y, Z_{max} and Z_{min} on the line
- Ex. 4
given $Z_L \rightarrow$ determine the distance to the max. and min. points of a standing wave
- Ex.8 given VSWR, short-circuit minima $\rightarrow Z_L$
- Ex.6 given $Z_L \rightarrow$ determine the relative λ position of load
- given a distance from the load \rightarrow determine the line impedance
- Ex.9 given $Z_L \rightarrow$ design a $\lambda/4$ transformer
- Ex.10, 11 given $Z_L \rightarrow$ design single- and double-stub tuners

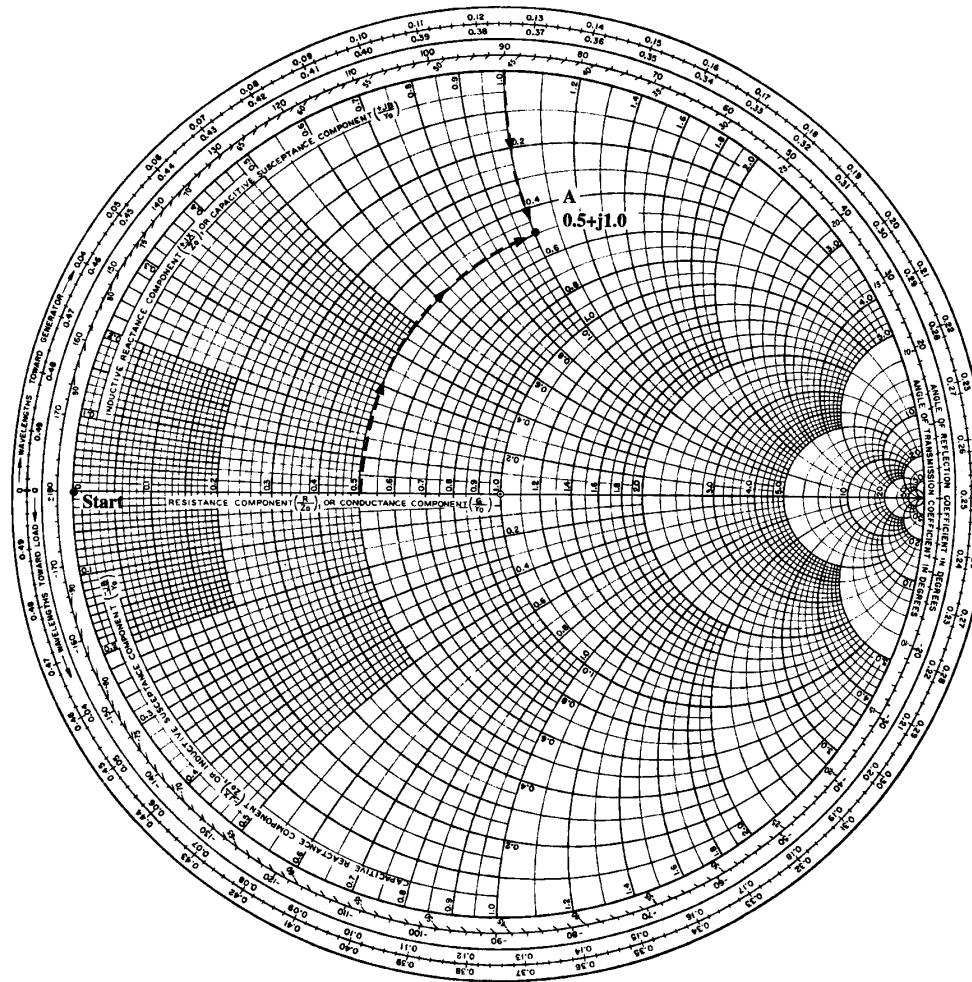2. Ex. 3.1 $Z_o=50\Omega$, plot $Z_L=25+j50\Omega$
 $z_L=0.5+j1$: A




3. Ex. 3.2 $Z_o=50\Omega$, $Z_L=50+j50\Omega$ find VSWR

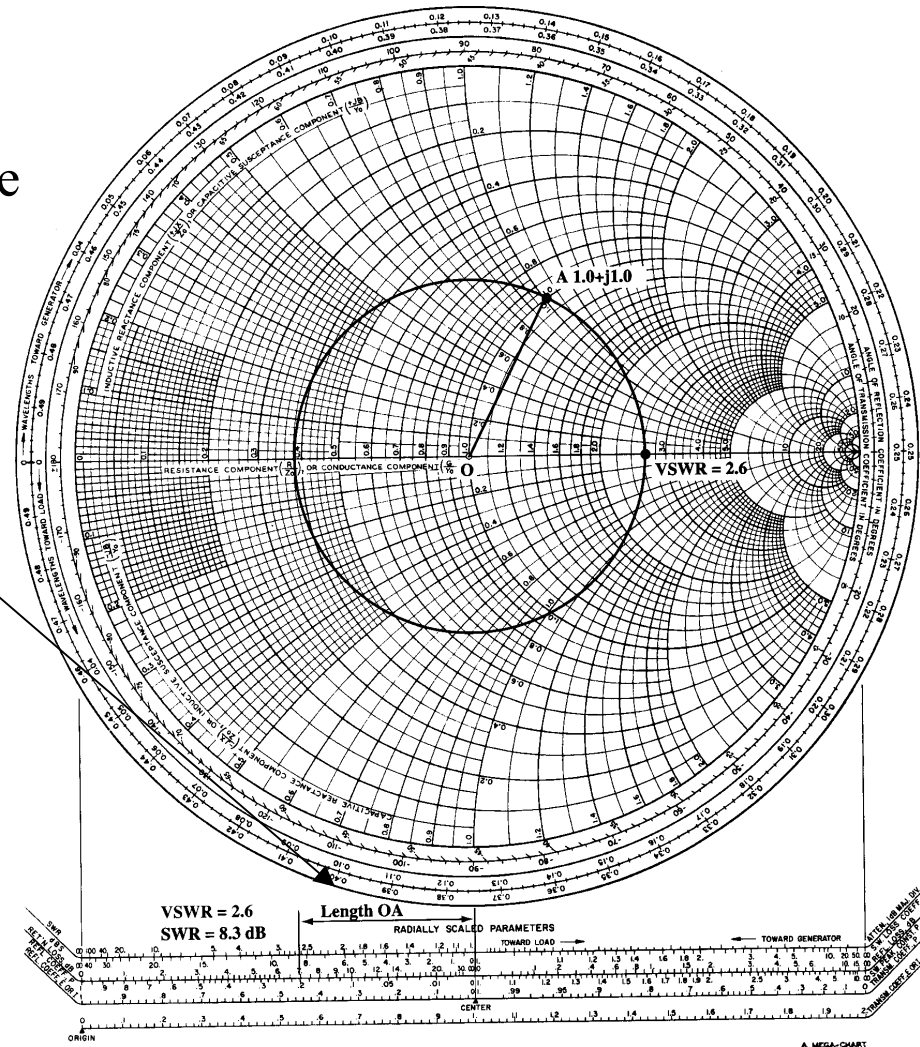- 1) $Z_L=1+j1 : A$
- 2) draw constant VSWR-circle
- 3) read $r_{\max}=2.6=\text{VSWR}$

or

read distance OA from
radially scaled parameters




4. Ex. 3.3 $Z_o=100\Omega$, $Z_L=100-j200\Omega$ find Γ

- 1) $Z_L=1-j2$: A
- 2) draw constant VSWR-circle
- 3) read distance OA from radially scaled parameters
 $|\Gamma|=0.71$
- 4) read phase -45°
- 5) read power reflection coefficient $0.5 = |\Gamma|^2$


reflection coefficient P

reflection coefficient E or I

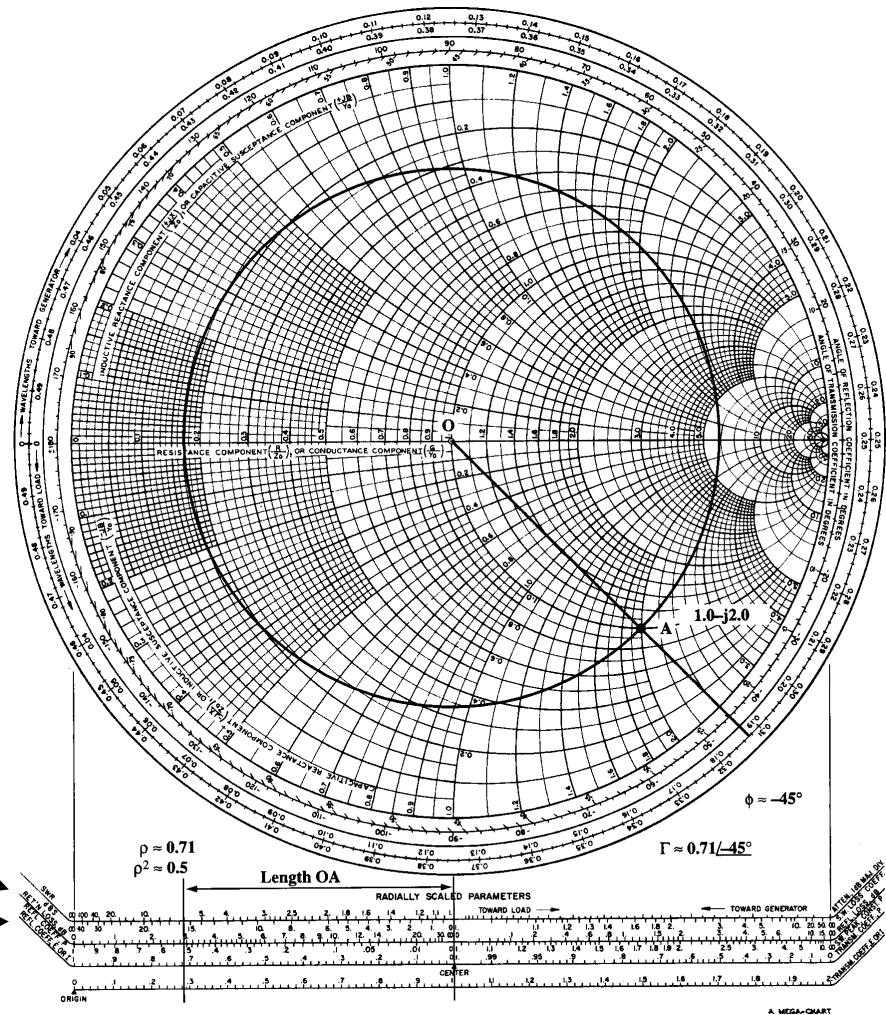


5. EX. 3.4 $Z_o=50\Omega$, $Z_L=100-j100\Omega$ find Z_{\max} and Z_{\min} on the line

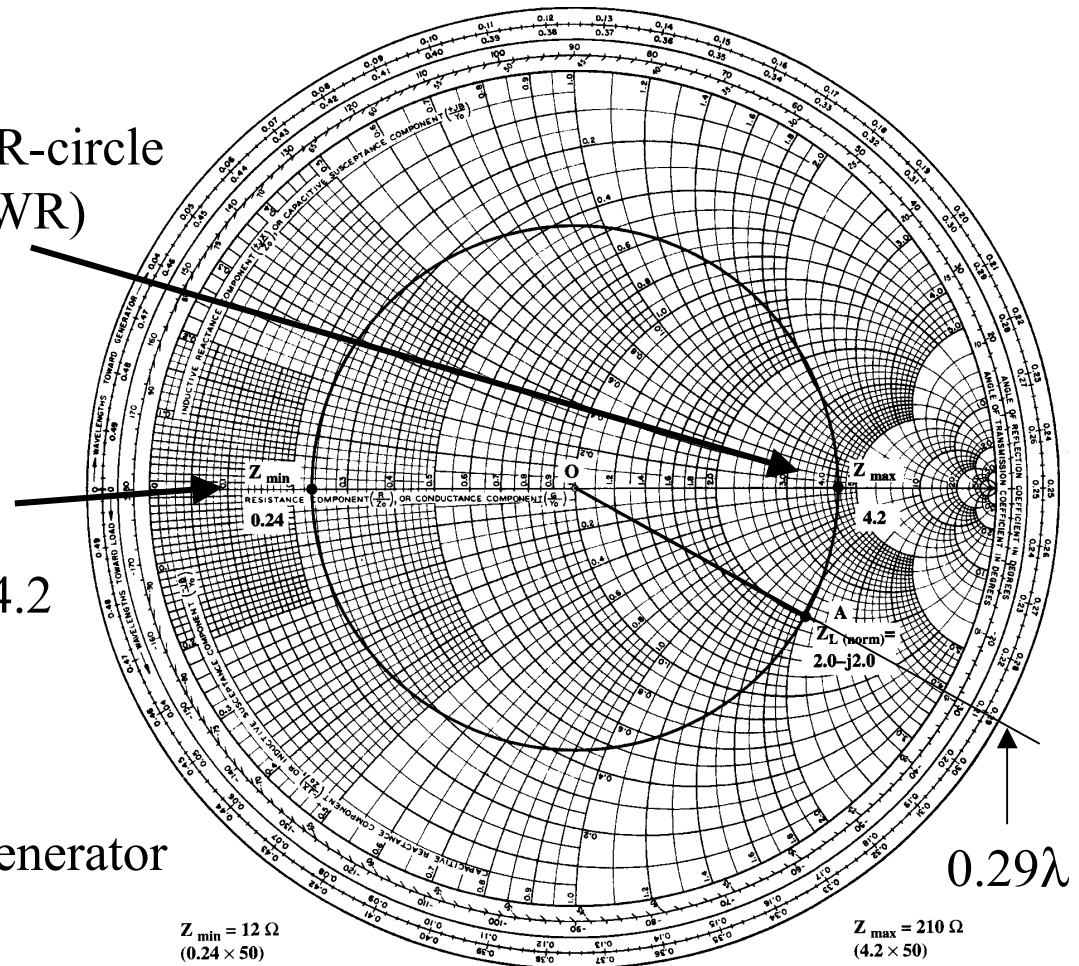- 1) $Z_L=2-j2$: A
- 2) draw constant VSWR-circle
- 3) read $Z_{\max}=4.2$ (=VSWR)
 $\rightarrow Z_{\max}=210\Omega$
 at 0.04λ toward load direction
 or at 0.46λ toward generator direction
- 4) read $Z_{\min}=0.24$ or $1/4.2$
 $\rightarrow Z_{\min}=12\Omega$
 at 0.21λ toward generator
 or at 0.29λ toward generator direction



6. Ex. 3.5 $Z_o=50\Omega$, $Z_L=50+j100\Omega$ find Y_L

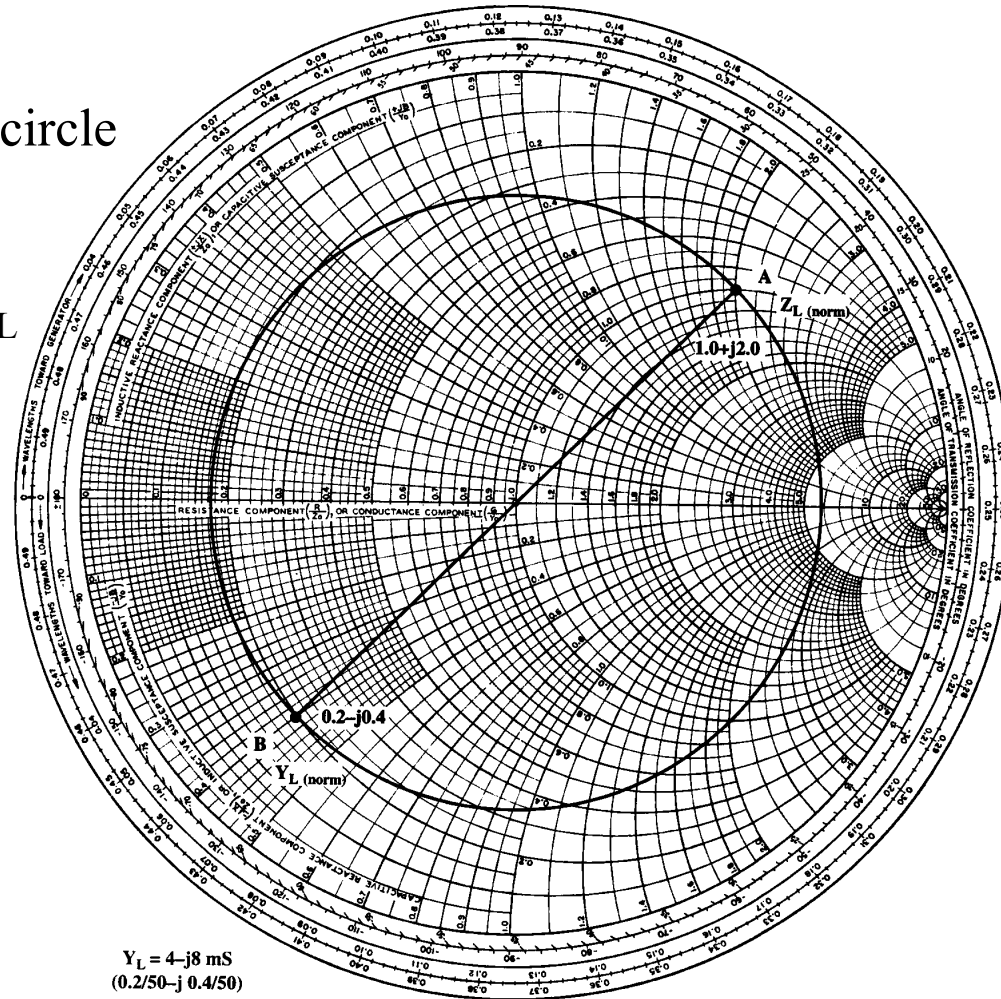- 1) $z_L=1+j2$: A
- 2) draw constant VSWR-circle
- 3) read B ($\lambda/4$ away)
 $y_L=0.2-j0.4$
- 4) $y_L=1/z_L = Z_o/Z_L = Z_o Y_L$
 $\rightarrow Y_L = y_L/Z_o$
 $= 0.004-j0.008S$




7. Ex. 3.6 $Z_o=50\Omega$, $Z_L=75+j75 \Omega$ find Z_L relative location

- 1) $Z_L=1.5+j1.5$: A
- 2) read location at 0.194λ toward generator


8. Ex. 3.7 Find Z_{in} at 0.2λ from the load

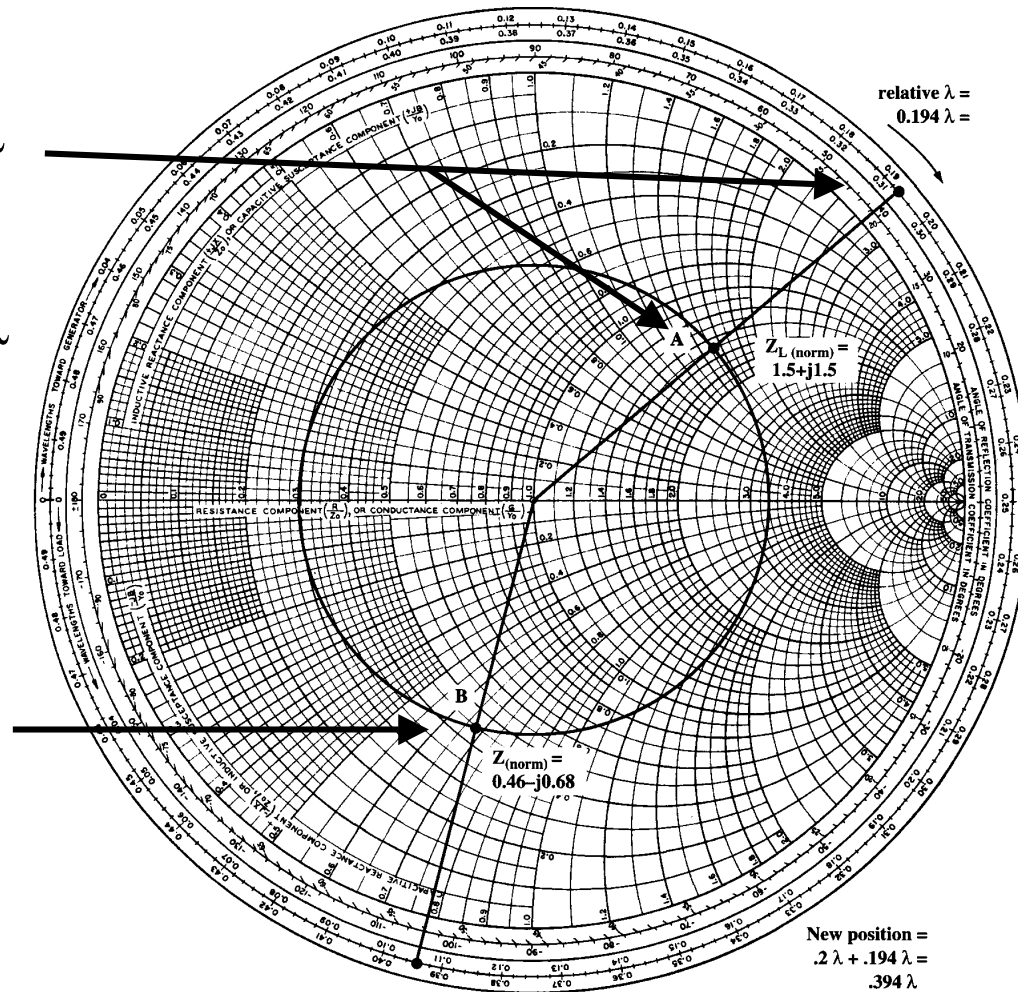- 1) draw constant VSWR circle
- 2) move 0.2λ toward generator (CW)
- 3) read B: $z = 0.46-j0.68$
 $\rightarrow Z_{in}=34.5-j51\Omega$



3.3 Short-circuit minima shift method

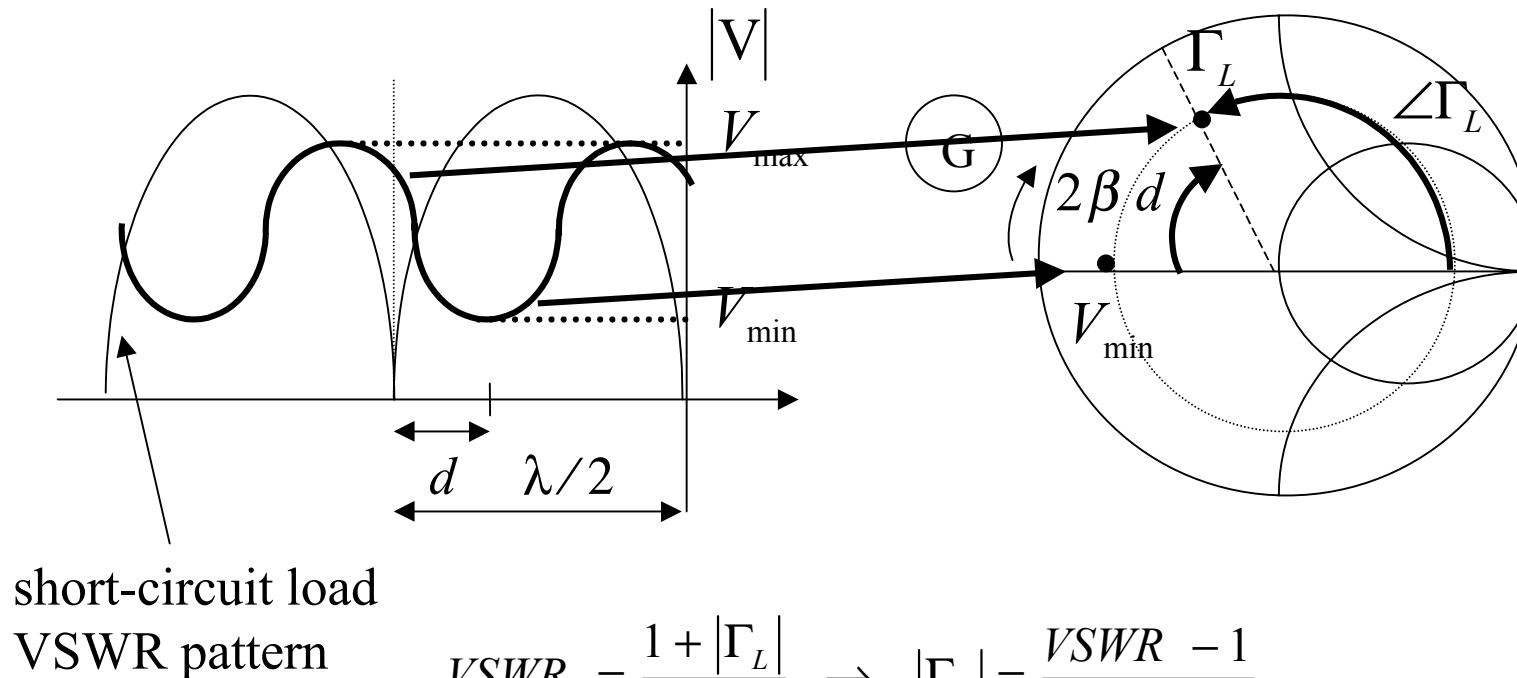1. given $VSWR$, distance minimum shifted $d \Rightarrow Z_L$



$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \rightarrow |\Gamma_L| = \frac{VSWR - 1}{VSWR + 1}$$

$$180^\circ - 2\beta d = 180^\circ(1 - 4d/\lambda) = \angle \Gamma_L$$

2. Ex. 3.8 $Z_0=50\Omega$, VSWR=2, short-circuit minima at 36.9mm and 55.2mm, load minima shifted to 42.9mm, find Z_L



$$\lambda = 2(55.2 - 36.9) = 36.6 \text{ mm}$$

$$d = 55.2 - 42.9 = 12.3 \text{ mm}$$

$$\angle \Gamma = 180(1 - 4 \times 12.3 / 36.6) = -62^\circ$$

$$Z_L = 1.1 - j0.75$$


$$Z_L = 55 - j37.5 \Omega$$

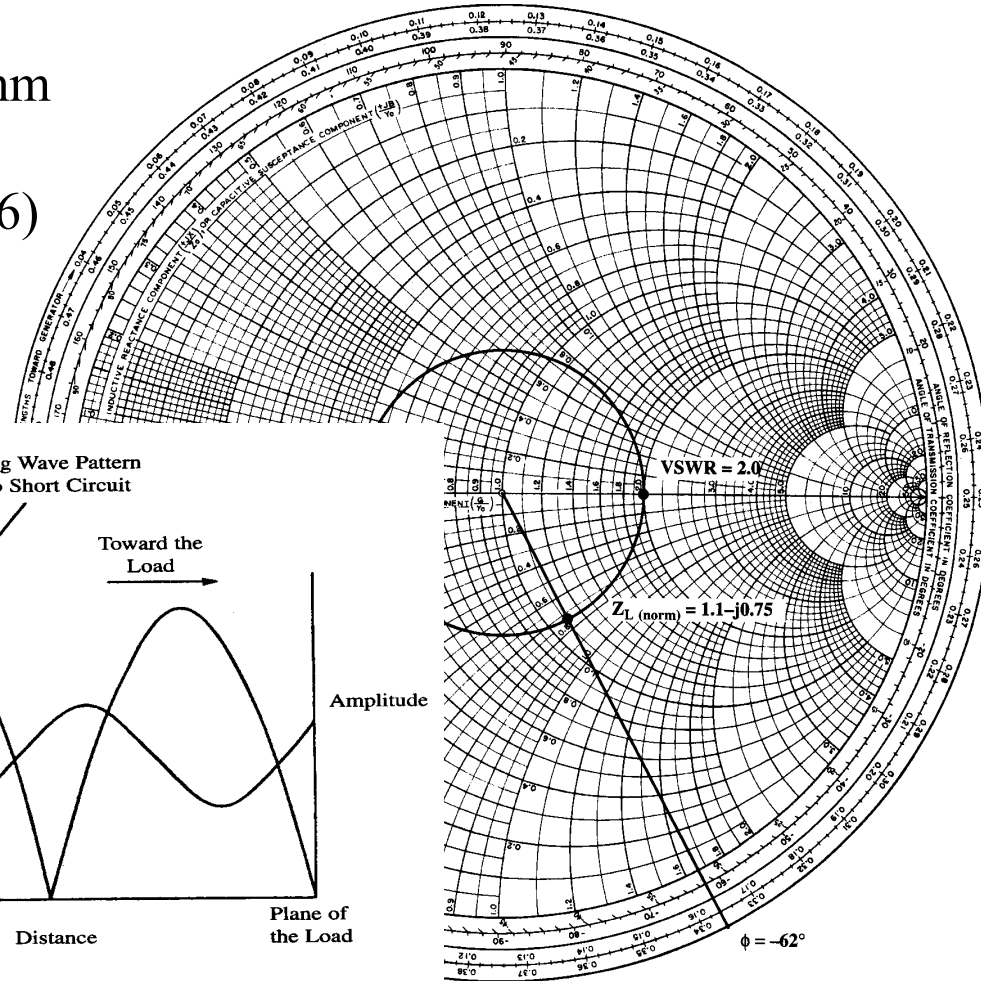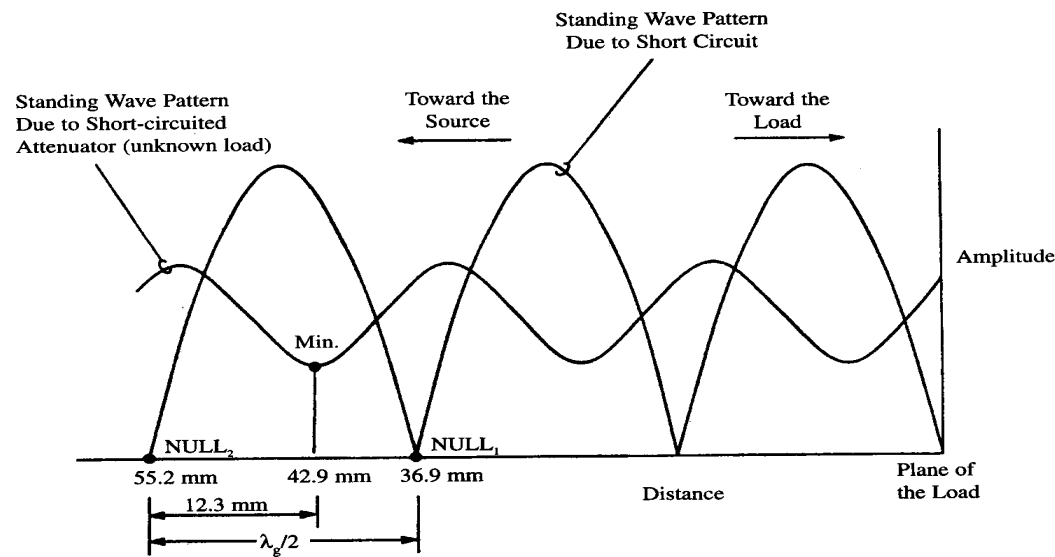

3.4 Impedance matching technique

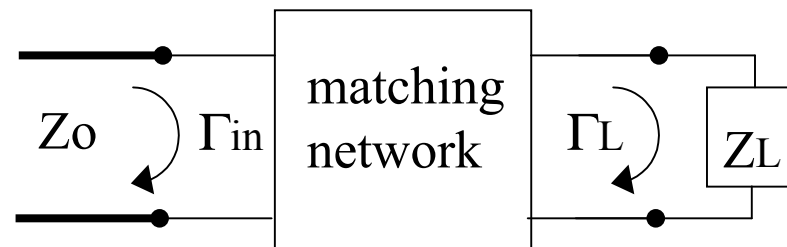1. Impedance matching concept

given Z_L , design a matching network to have $\Gamma_{in} = 0$ or selected Γ_{in} value




2. Matching network usually uses lossless elements: L, C, transmission line, transformer,...for a narrow bandwidth match.
3. Lossy matching elements, e.g. resistive pad, can give a broadband match, but degrades the circuit efficiency.
4. There are ∞ possible solutions.
5. Use Smith chart to find the optimal design.

3.4 Impedance matching technique

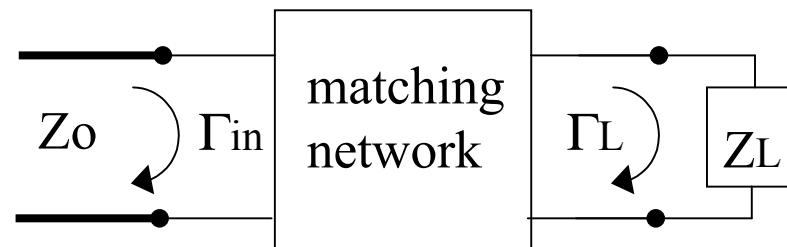
1. Impedance matching concept

given Z_L , design a matching network to have $\Gamma_{in} = 0$ or selected Γ_{in} value




2. Matching network usually uses lossless elements: L, C, transmission line, transformer,...for a narrow bandwidth match.
3. Lossy matching elements, e.g. resistive pad, can give a broadband match, but degrades the circuit efficiency.
4. There are ∞ possible solutions.
5. Use Smith chart to find the optimal design.

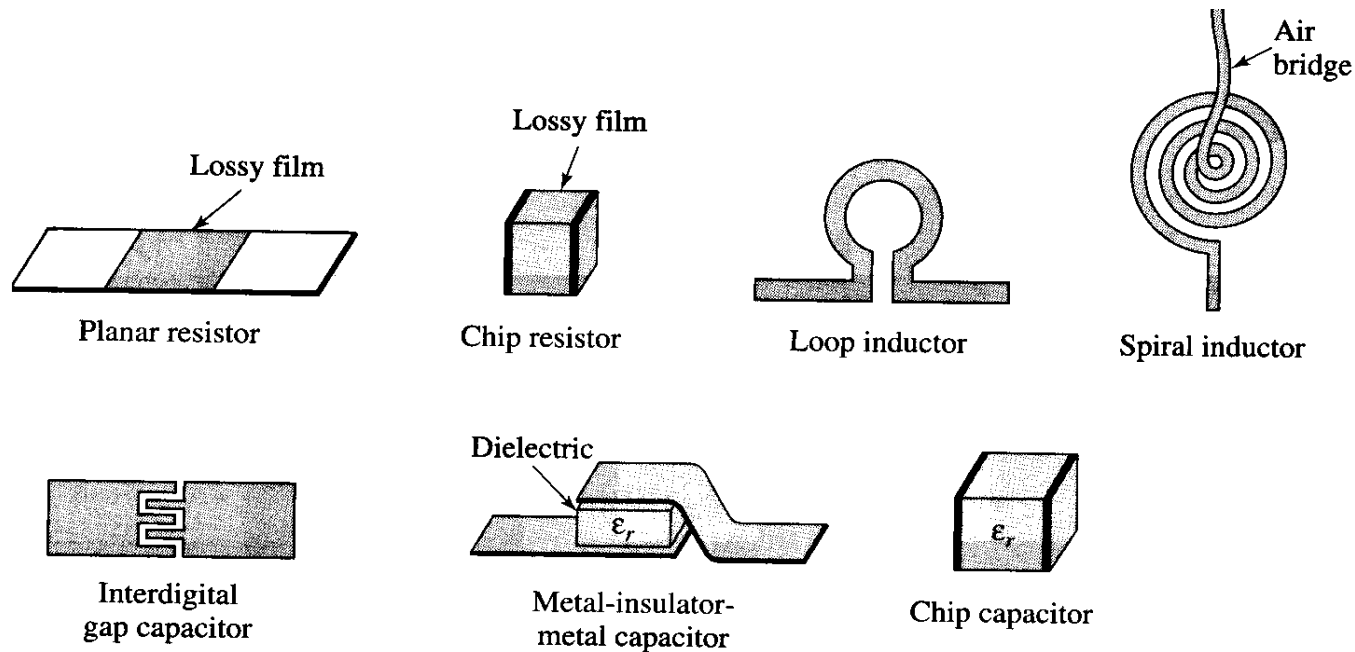6. Factors for selecting matching circuit: complexity, bandwidth, implementation and adjustability
7. Lumped elements ($\text{size} < \lambda/10$) for microwave circuits
capacitor: chip capacitor, MIM capacitor ($< 25\text{pF}$), interdigital gap capacitor ($< 0.5\text{pF}$), open stub ($< 0.1\text{pF}$)
inductor: chip inductor, loop inductor, spiral inductor ($< 10\text{nH}$)
resistor: chip resistor, planar resistor



8. $\lambda/4$ transformer

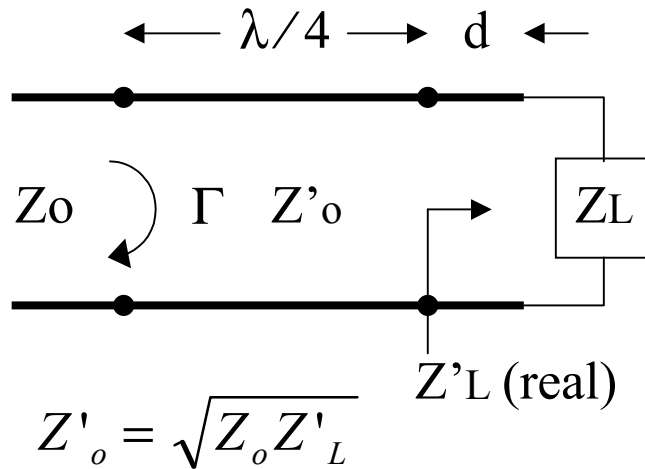


9. Ex. 3.9 $Z_o = 300\Omega$,
 $Z_L = 250 + j450\Omega$

1) $Z_L = 0.83 + j1.5 : A$

2) draw constant Γ -circle
 3) move toward generator
 B: $r = 4.75$, $d = 0.08\lambda$

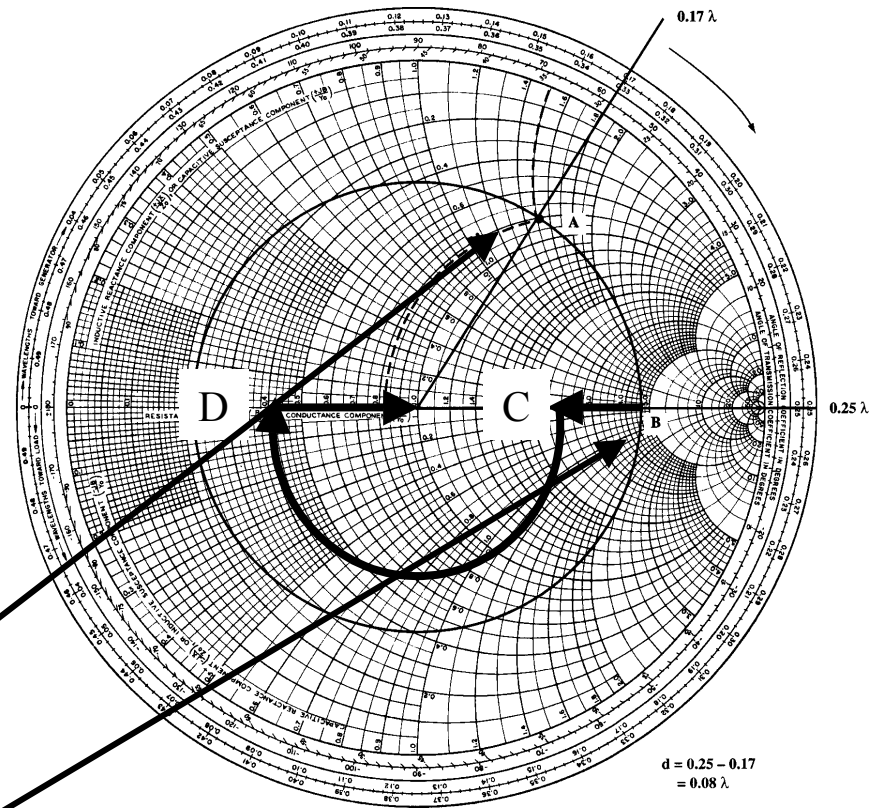4) $Z'_o = \sqrt{300 \times 4.75 \times 300}$
 $= 654\Omega$







5) normalize to 654Ω
 $4.75 \times 300 / 654 = 2.18 : C$
 moves 180° CW to D: 0.46
 normalize to 300Ω
 $0.46 \times 654 / 300 = 1$





10. open-circuit stub $Z_{in} = \frac{Z_o}{j \tan \beta l} \equiv \frac{1}{j \omega C}$

short-circuit stub $Z_{in} = jZ_o \tan \beta l \equiv j \omega L$



11. Series stub

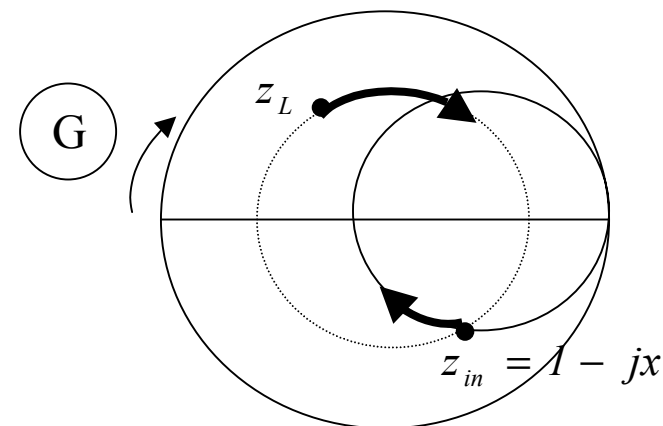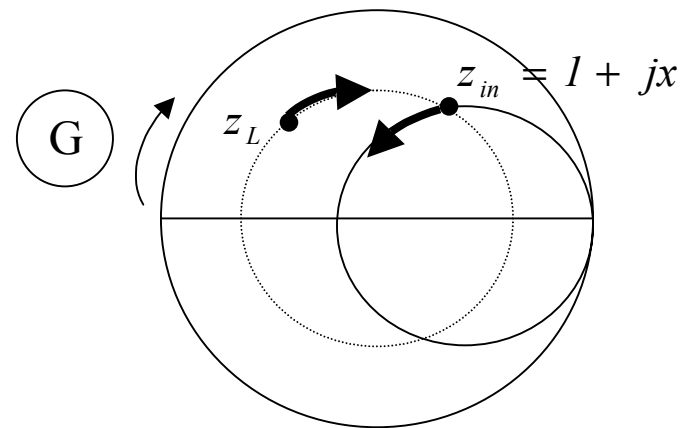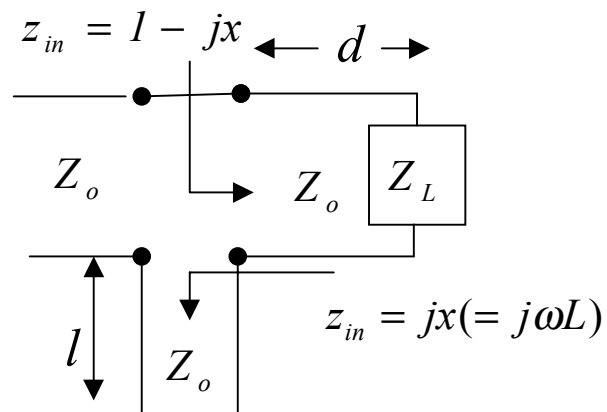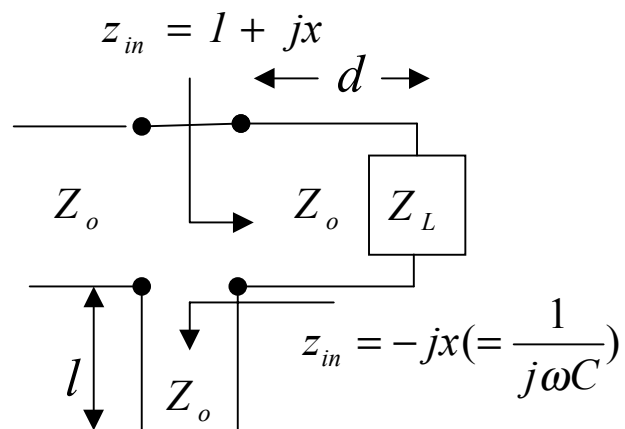

12. Shunt stub

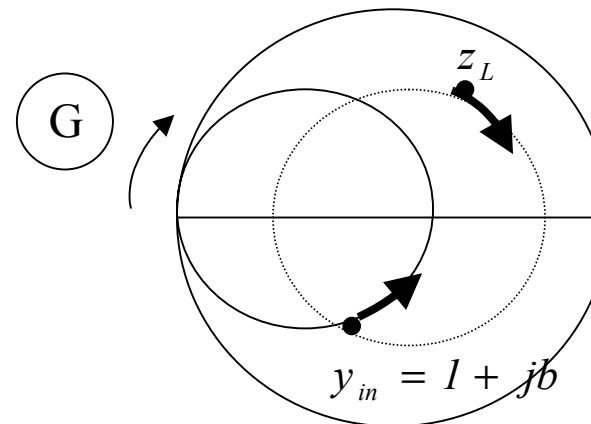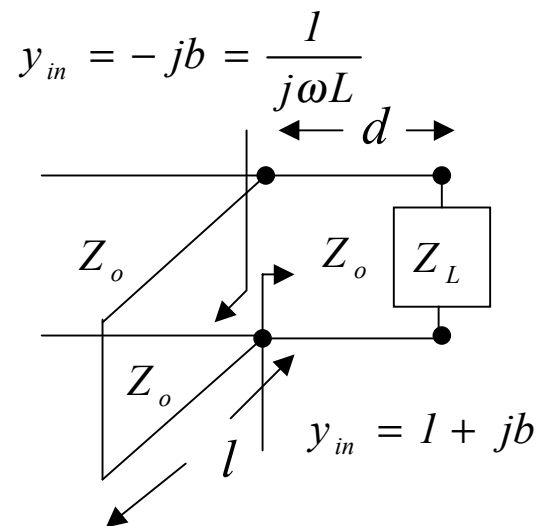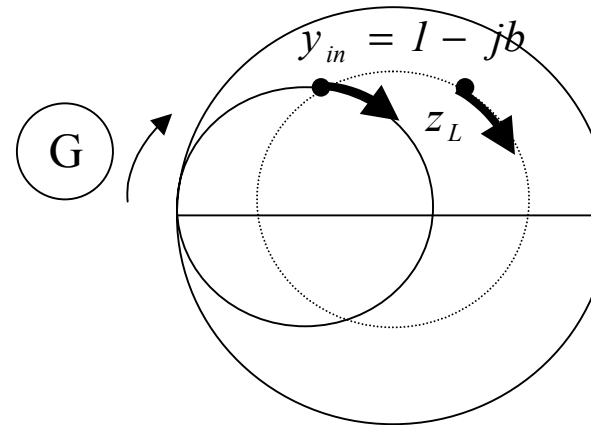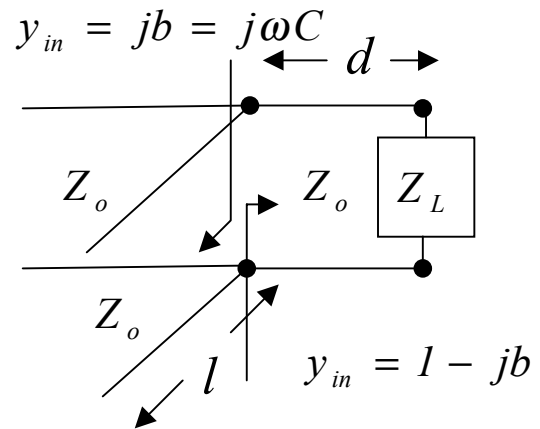

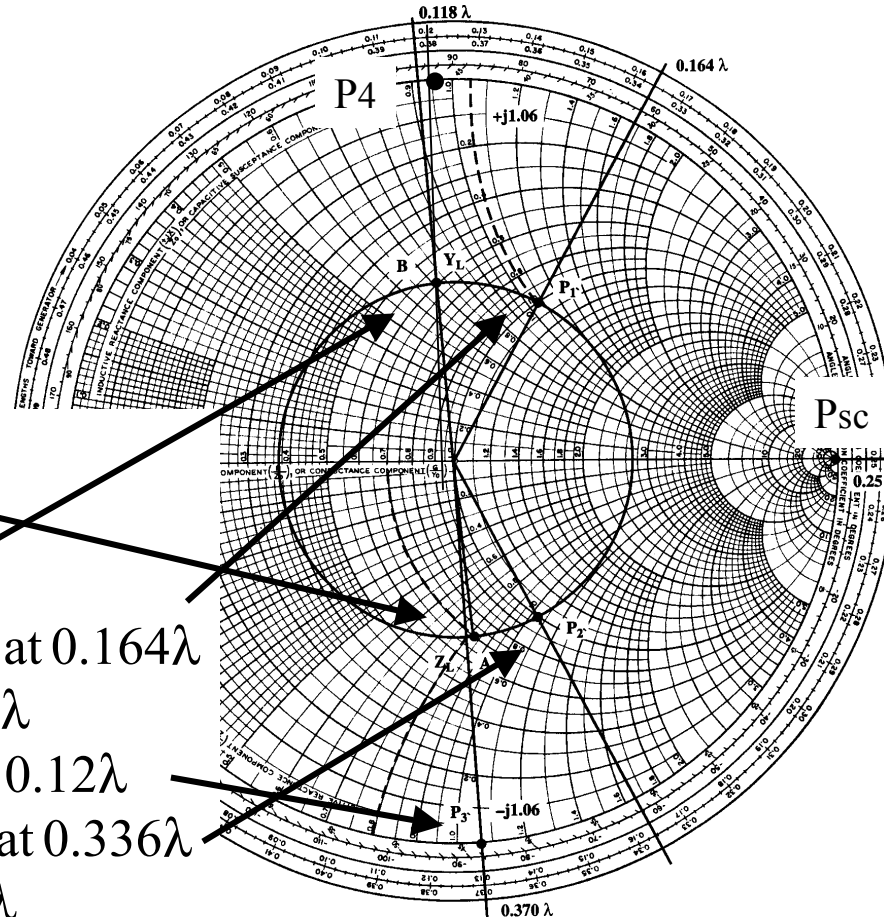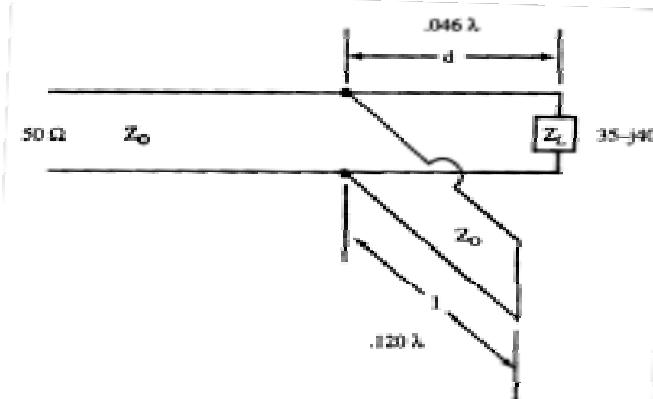
13. Ex. 3.10 $Z_o=50\Omega$, $Z_L=35-j40\Omega$, find d and l for a short-circuit single stub




- 1) $Z_L=0.7-j0.8$:A
- 2) draw constant VSWR circle
- 3) locate y_L : B at 0.118λ
- 4) move CW to P_1 : $y=1+j1.06$ at 0.164λ
 $\rightarrow d_1=0.164\lambda-0.118\lambda=0.046\lambda$
 $\rightarrow P_3$: $-j1.06$ at $0.37\lambda \rightarrow l_1=0.12\lambda$
- 5) move CW to P_2 : $y=1-j1.06$ at 0.336λ
 $\rightarrow d_2=0.336\lambda-0.118\lambda=0.218\lambda$
 $\rightarrow P_4$: $j1.06$ at $0.12\lambda \rightarrow l_2=0.37\lambda$
 \rightarrow longer line \rightarrow narrower bandwidth

14. Ex. 3.11 $Z_0=50\Omega$, $Z_L=100+j60\Omega$, find d and l for a short-circuit single stub at 1GHz with $v_f=0.95$.

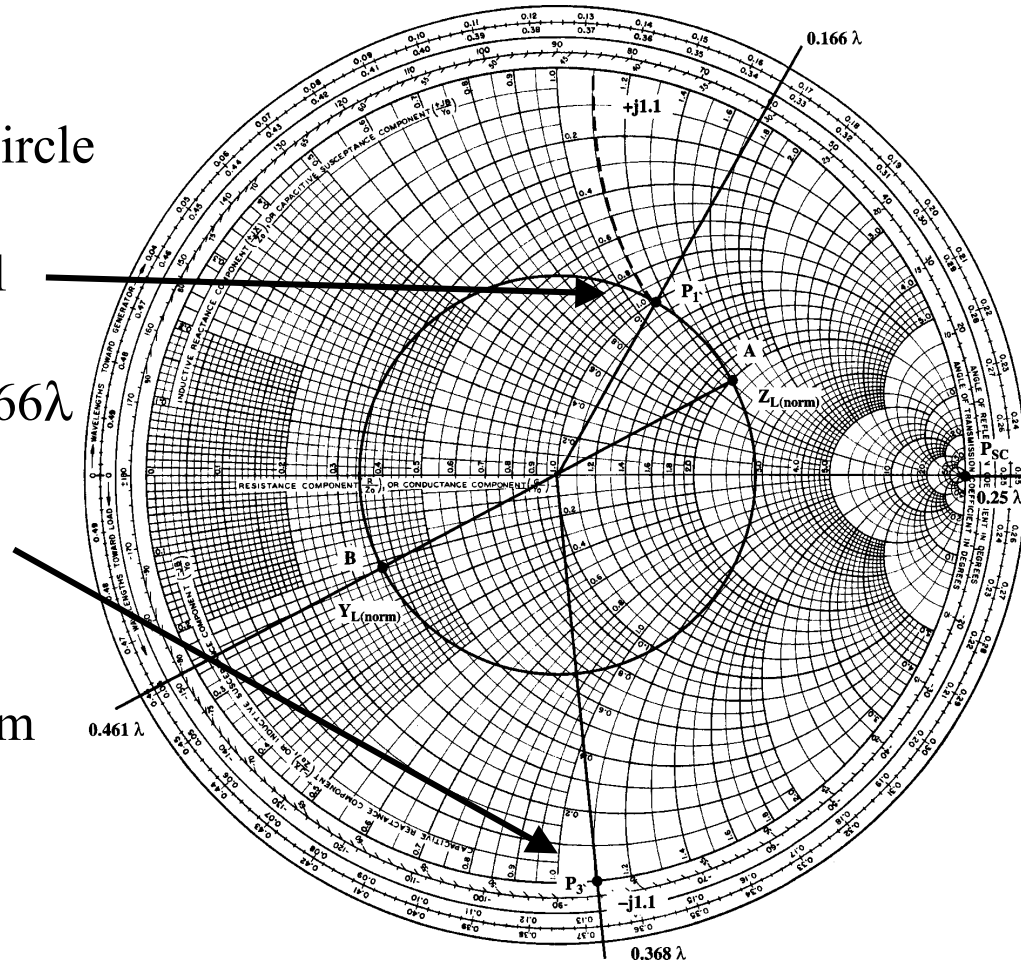- 1) $Z_L=2+j1.2 : A$
- 2) draw constant VSWR circle
- 3) locate $y_L : B$ at 0.461λ
- 4) move CW to $P_1 : 1+j1.1$
at 0.166λ
→ $d = 0.5\lambda - 0.461\lambda + 0.166\lambda$
 $= 0.205\lambda$
→ $P_3 : -j1.1$ at 0.368λ
→ $l = 0.368\lambda - 0.25\lambda$
 $= 0.118\lambda$
- 5) $\lambda = 0.95 \times c / 1\text{GHz} = 28.5\text{cm}$
 $d = 5.8\text{cm}$, $l = 3.36\text{cm}$



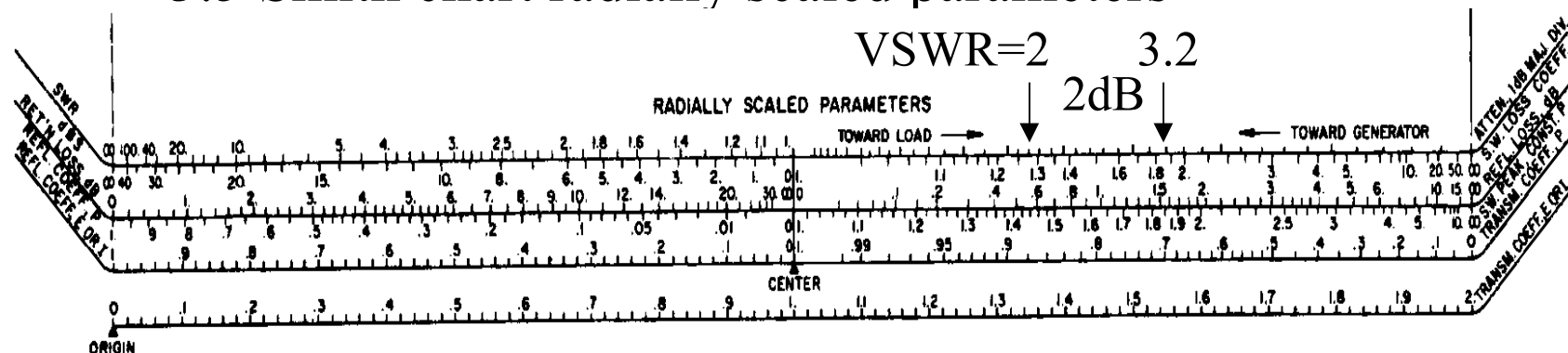3.5 Smith chart radially scaled parameters



1. reflection: REFL. COEF. E or I $0 \leq |\Gamma| \leq 1$, P $0 \leq |\Gamma|^2 \leq 1$
 RET'N LOSS (dB) $0 \leq -20 \log |\Gamma| \leq \infty$
 REFL. LOSS (dB) $0 \leq -10 \log(1 - |\Gamma|^2) \leq \infty$
2. transmission loss: TRANSM. COEF. E or I, P, S.W. LOSS COEF.,
 ATTEN. 1dB for lossy line
3. SWR: $1 \leq VSWR \leq \infty$, $0 \leq VSWR(\text{dB}) \leq \infty$
4. Ex. A lossy 50Ω line has 2dB attenuation. If $VSWR=2$ at input,
 find VSWR at load end.

$$VSWR=2 \rightarrow \text{ATTEN} + 2\text{dB}$$

$$\rightarrow VSWR=3.2$$

Homework #3 (due 2 weeks)
 Chap.3: problems 1-14